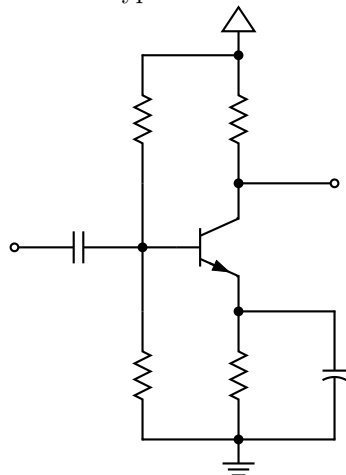


Here's a typical transistor-based audio amplifier.



Since the transistor is intended to operate in its active region throughout the signal cycle, this is a Class A amplifier.